

EXPERIMENT NO. 4

AIM OF THE EXPERIMENT:

Investigation of BJT in CE configuration and sketch its input and output characteristics.

EQUIPMENTS and COMPONENTS REQUIRED:

Sl. No	Name	Specification
1	Transistor	BC 547
2	Resistors	10kΩ, 1kΩ
3	Variable resistors	100k, 1k
4	Voltmeter	(0-10)V- 2 Nos.
5	Ammeter	(0-200)μA & (0-10) mA
6	Bread Board	
7	Connecting wire	

CIRCUIT DIAGRAM:

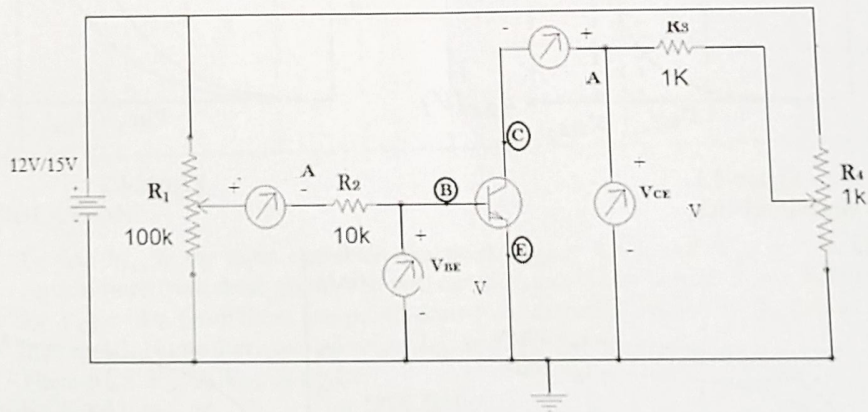


Figure.4 (Circuit diagram for CE configuration)

THEORY:

The transistor is a two port device. Its input circuit contains a dependent voltage source in series with impedance and output circuit contains a dependent current source in parallel with impedance. Define by the relations as shown below:

$$V_{be} = h_{ie}I_b + h_{re}V_{ce} \text{----- (1)}$$

$$I_c = h_{fe}I_b + h_{oe}V_{ce} \text{----- (2)}$$

From equation (1) $h_{ie} = V_{be}/I_b|V_{ce} = 0$, Input impedance with output short-circuit.

$h_{re} = V_{be}/V_{ce}|I_b = 0$, Reverse open circuit voltage gain.

These two parameters h_{ie} and h_{re} can be found from the input characteristics.

From the Fig:4.1, $h_{ie} = V_{be}/I_b|V_{CE} = \text{constant}$

and from Fig: 4.2, $h_{re} = V_{be}/V_{ce}|I_B = \text{constant}$

From equation (2) $h_{fe} = I_c/I_b|V_{ce} = 0$, Forward short circuit current gain.

$h_{oe} = I_c/V_{ce}|I_b = 0$, Output admittance with input open-circuited.

These two parameters h_{fe} and h_{oe} can be found from the output characteristics.

From the Fig:4.3, $h_{fe} = I_c/I_b|V_{CE} = \text{constant}$

and from Fig:4.4, $h_{oe} = I_c/V_{ce}|I_B = \text{constant}$

Input characteristics:

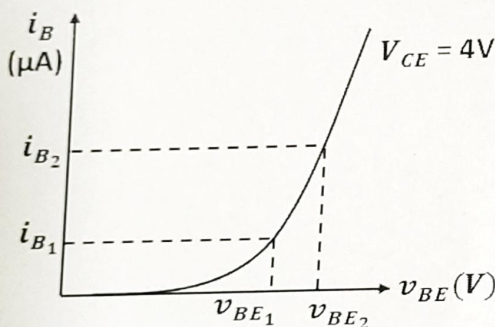


Figure.4.1

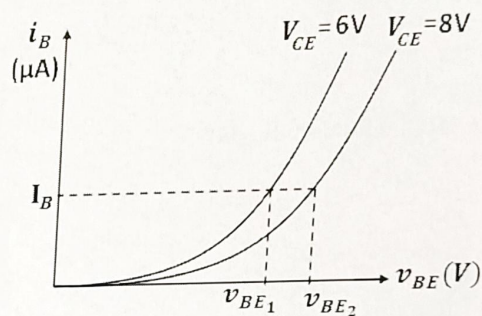


Figure.4.2

Output characteristics:

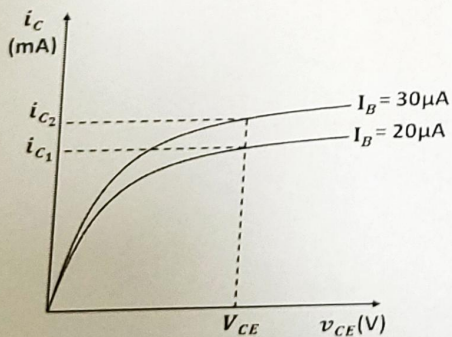


Figure.4.3

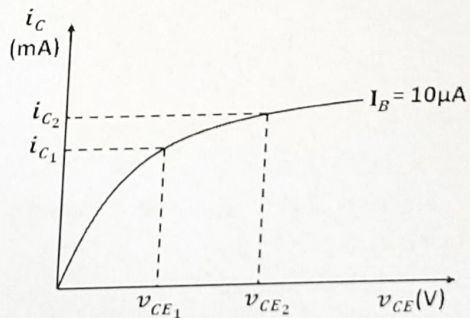


Figure.4.4

PROCEDURE:

1. Make the connection as per circuit diagram.

For the input characteristics:

2. Set $V_{CE} = 4v$ by adjusting R_4 .
3. Varying R_1 , note the values of I_B and V_{BE} , so that $V_{CE} = 4v$ always (adjust R_4 for each set of I_B and V_{BE}).
4. Repeat this for the values of $V_{CE} = 6v$ and $8v$.

For the output characteristics:

5. Set $I_B = 10\mu A$, by adjusting R_1 .
6. Varying R_4 note the values of I_C and V_{CE} .
7. Repeat this for the values of $I_B = 20\mu A$ and $30\mu A$.
8. Draw the graph between I_B and V_{BE} for the input characteristics, and between I_C and V_{CE} for the output characteristics.

TABULATION:

$V_{CE} = 4v$		$V_{CE} = 6v$		$V_{CE} = 8v$		$I_B = 10\mu A$		$I_B = 20\mu A$		$I_B = 30\mu A$	
I_B	V_{BE}	I_B	V_{BE}	I_B	V_{BE}	I_C	V_{CE}	I_C	V_{CE}	I_C	V_{CE}

CALCULATION:

1. To find h_{ie} , in the input characteristics mark $V_{BE} = 0.5 V$ and $V_{BE} = 1 V$. Draw two vertical lines from these points that will cut the input characteristic at two different points for $V_{CE} = 4v$. From these two points draw two horizontal lines to the I_B axis as shown in the Fig:4.1. Name these two points as I_{B1} and I_{B2} .

Then, $h_{ie} = V_{be}/I_b|V_{CE} = 4v$ i.e.

$$h_{ie} = \Delta v_{BE} / \Delta i_B | V_{CE} = \text{constant} = \frac{v_{BE2} - v_{BE1}}{i_{B2} - i_{B1}} | V_{CE} = \text{constant}$$

2. To find h_{re} , in the input characteristics draw a horizontal line from I_B axis. It will cut the characteristics for $V_{CE} = 6v$ and $8v$ at two points. From these two points draw two vertical lines to the V_{BE} axis, mark as V_{BE1} and V_{BE2} .

Then, $h_{re} = V_{be}/V_{ce}|I_B = \text{constant}$ i.e.

$$h_{re} = \Delta v_{BE} / \Delta v_{CE} | I_B = \text{constant} = \frac{v_{BE2} - v_{BE1}}{v_{CE2} - v_{CE1}} | I_B = \text{constant}$$

3. To find h_{oe} , in the output characteristics mark $V_{CE} = 3.0 V$ and $V_{CE} = 6.0 V$. Draw two vertical lines from these points that will cut the output characteristic at two different points for $I_B = 10\mu A$. From these two points draw two horizontal lines to the I_C axis as shown in the Fig:4.4. Name these two points as I_{C1} and I_{C2} .

Then, $h_{oe} = I_c/V_{ce}|I_B = 10\mu A$ i.e.

$$h_{oe} = \Delta i_c / \Delta v_{ce} | I_B = \text{constant} = \frac{i_{c2} - i_{c1}}{v_{ce2} - v_{ce1}} | I_B = \text{constant}$$

4. To find h_{fe} , in the output characteristics draw a vertical line from V_{ce} axis. It will cut the characteristics for $I_B = 20\mu A$ and $I_B = 30\mu A$ at two points. From these two points draw two horizontal lines to the I_c axis, mark as I_{c1} and I_{c2} .

Then, $h_{fe} = I_c/I_b|V_{ce} = \text{constant}$ i.e.

$$h_{fe} = \Delta i_c / \Delta i_b | V_{ce} = \text{constant} = \frac{i_{c2} - i_{c1}}{i_{b2} - i_{b1}} | V_{ce} = \text{constant}$$

CONCLUSION:

(To be written by students after the experiment)